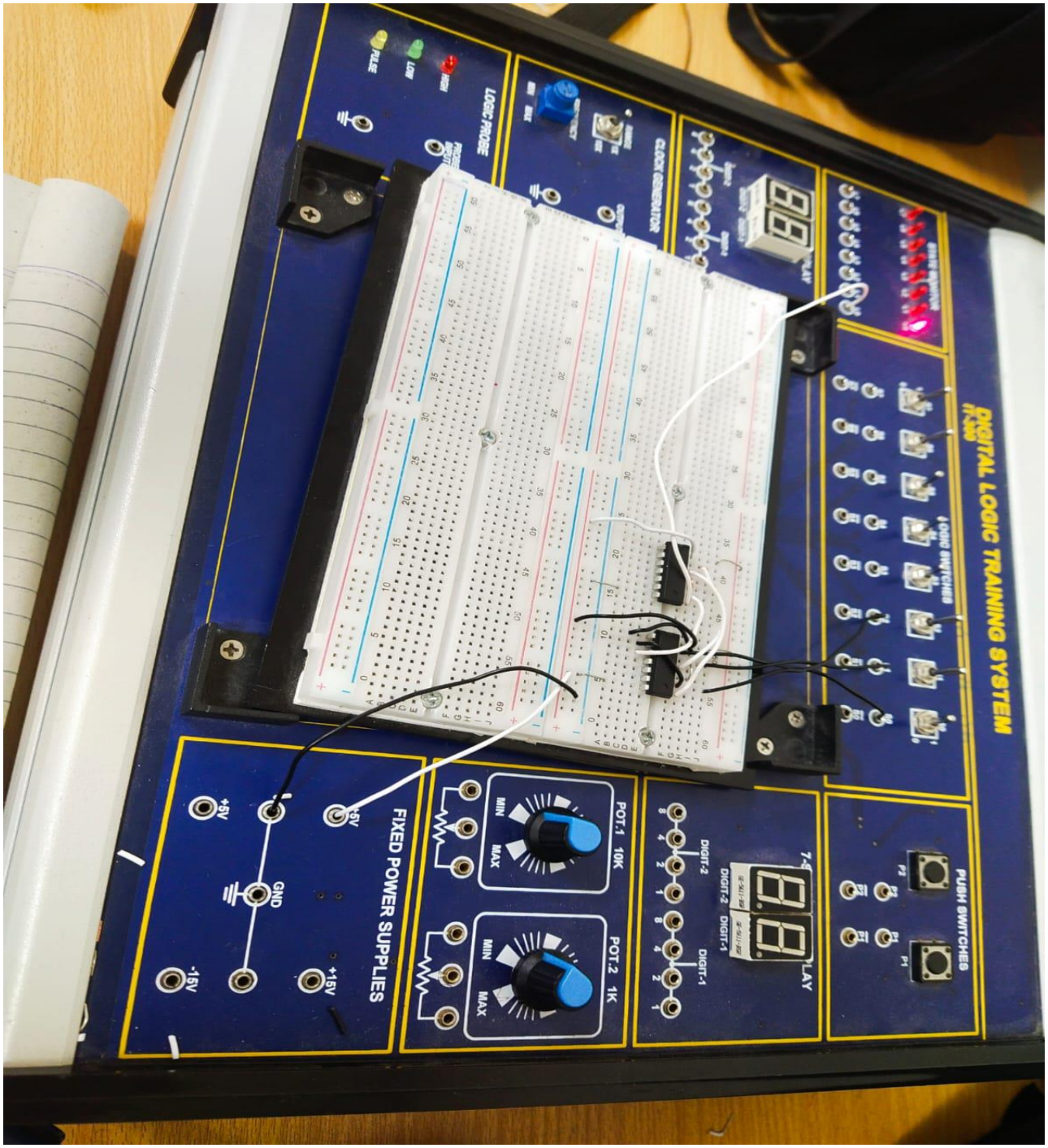
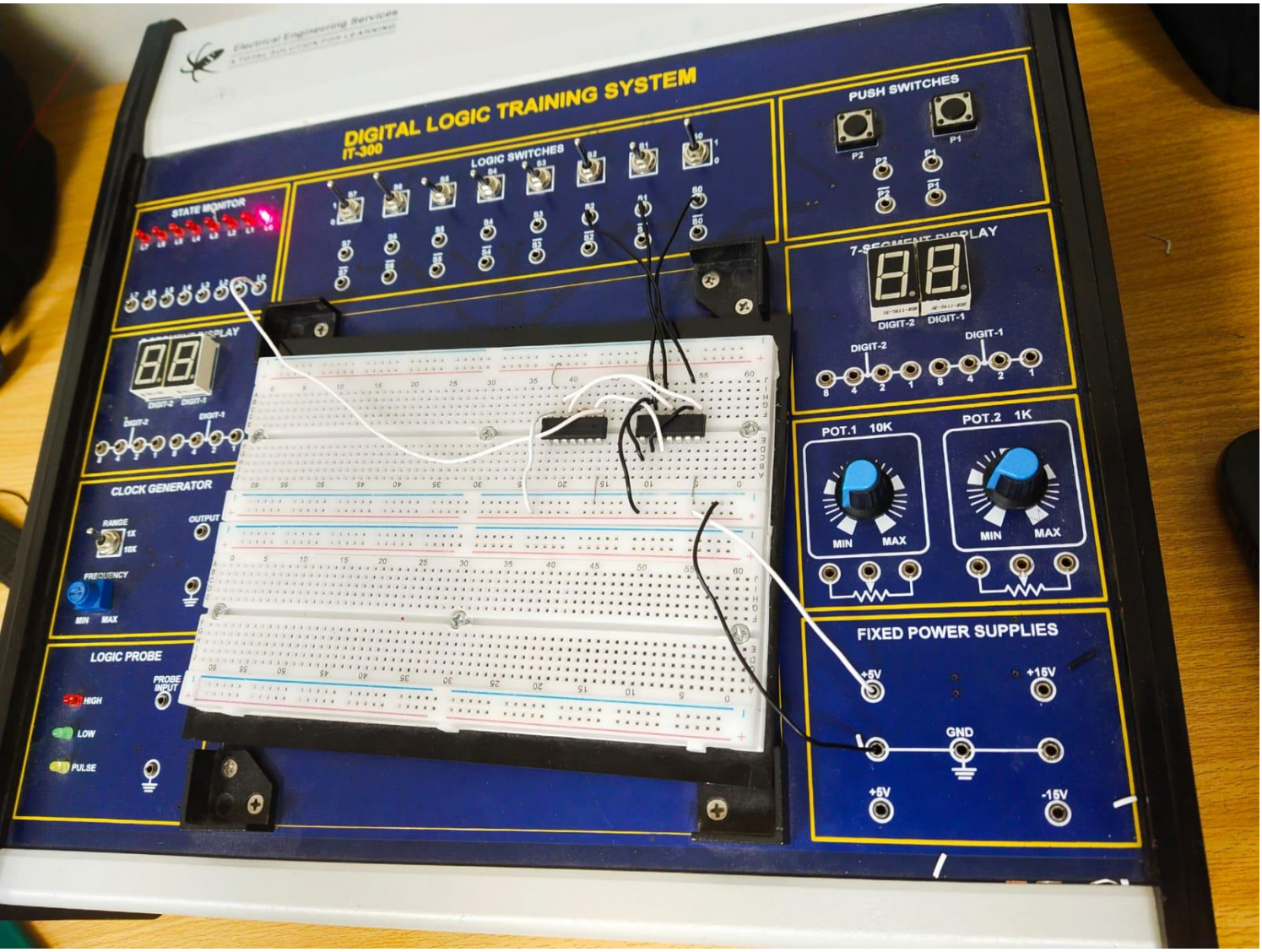
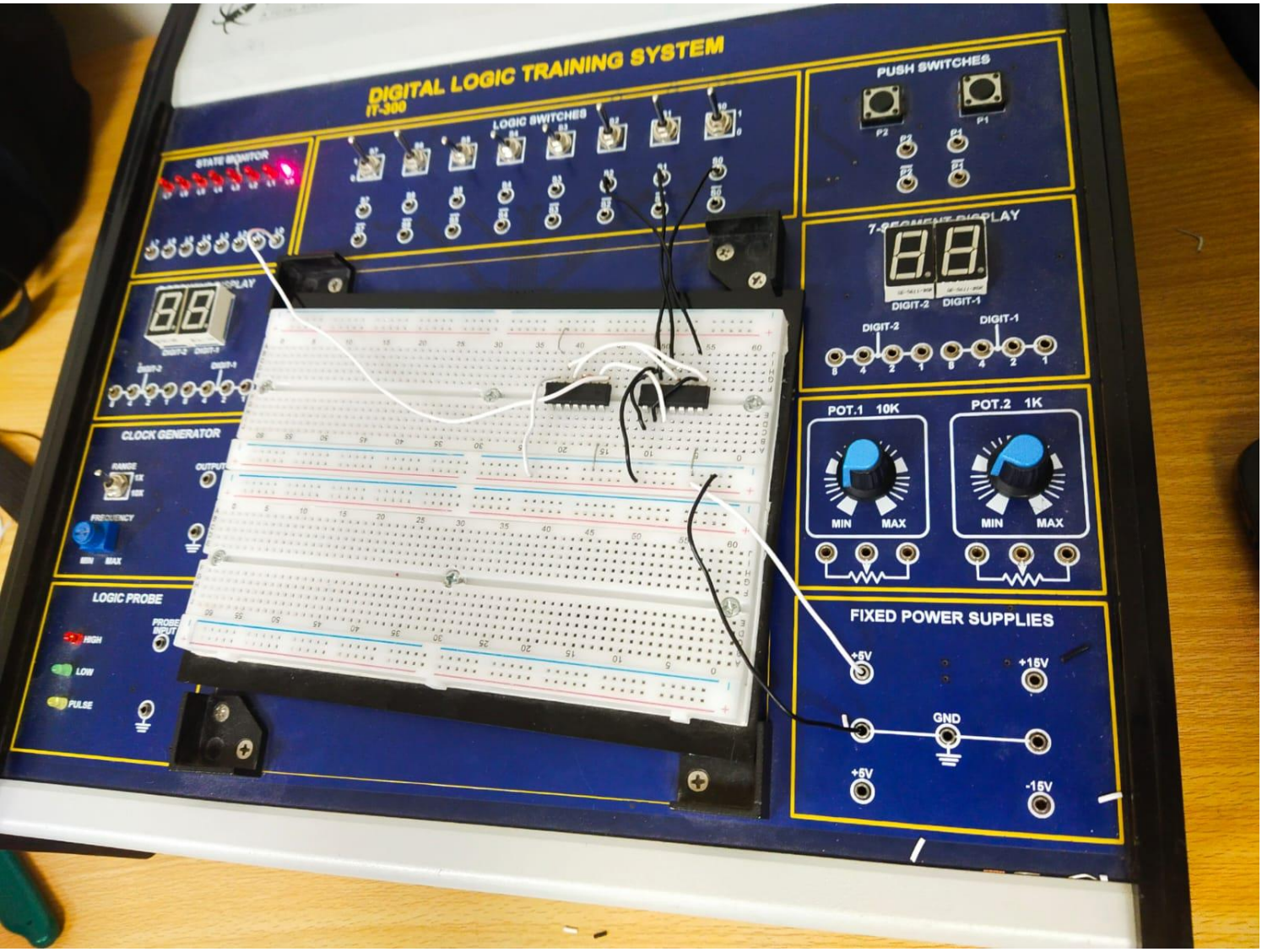
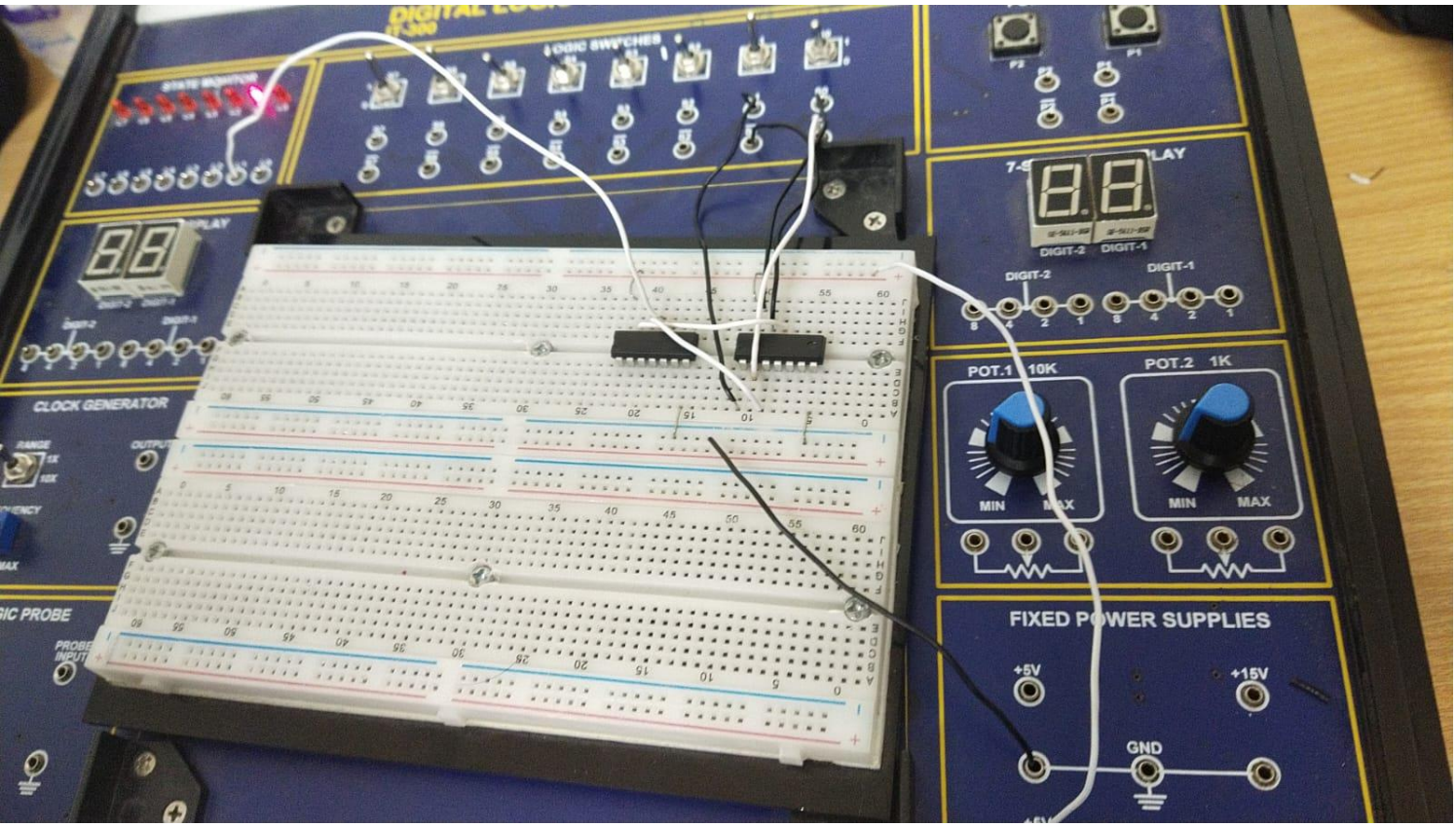
TASK #01

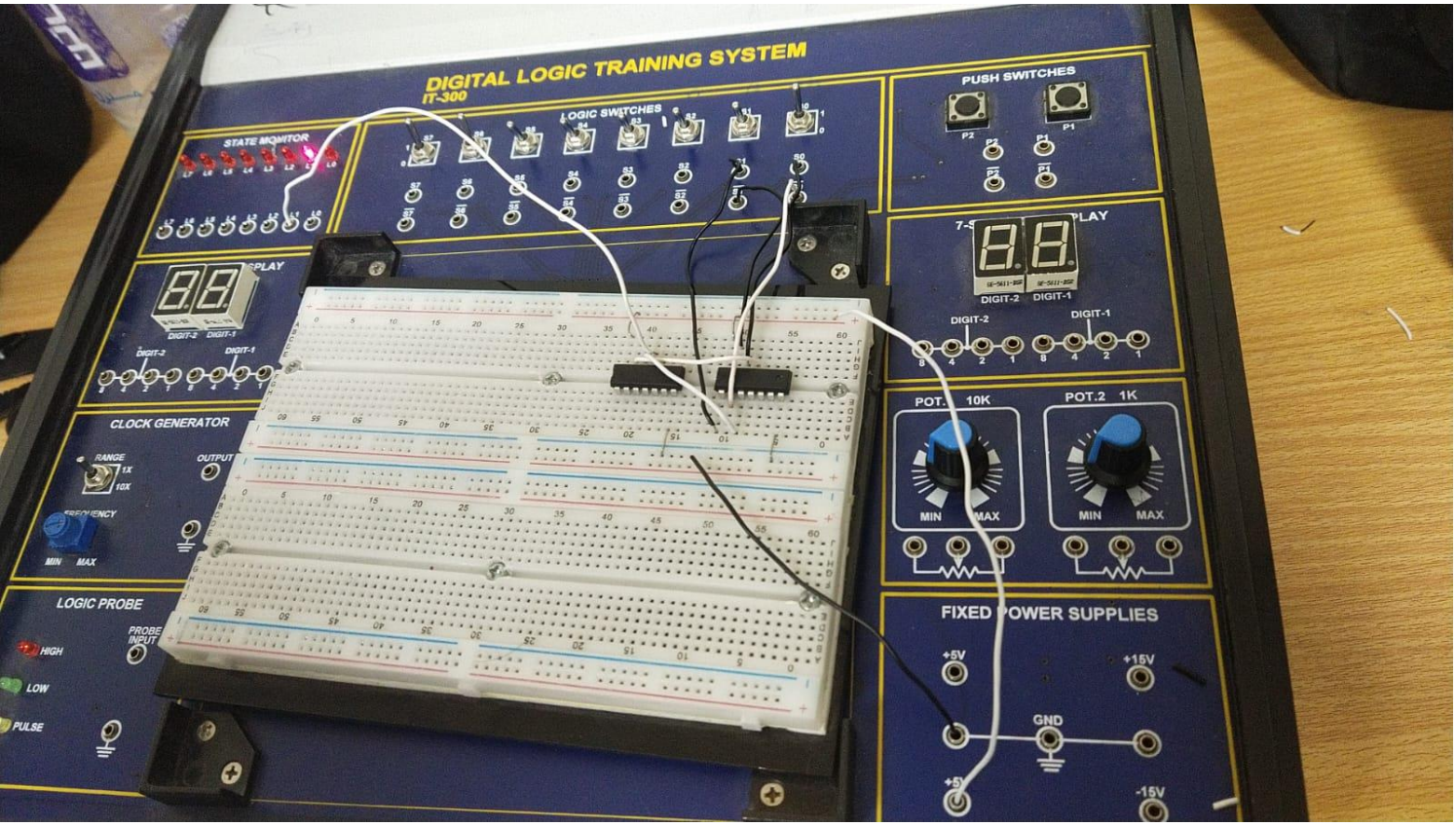

DIGITAL LOGIC TRAINING SYSTEM
LOGIC PROBE
CLOCK GENERATOR
FIXED POWER SUPPLIES
+5V
GND
-15V
+15V
POT.1 10K
POT.2 1K
MIN
MAX
DIGIT-2
DIGIT-1
PUSH SWITCHES
P3
P2
P1
P0


DIGITAL LOGIC TRAINING SYSTEM
IT-300
LOGIC SWITCHES
PUSH SWITCHES
STATE MONITOR
7-SEGMENT DISPLAY
DIGIT-2
DIGIT-1
CLOCK GENERATOR
RANGE
OUTPUT
FREQUENCY
MIN
MAX
POT.1 10K
POT.2 1K
LOGIC PROBE
PROBE INPUT
HIGH
LOW
PULSE
FIXED POWER SUPPLIES
+5V
+15V
GND
-15V

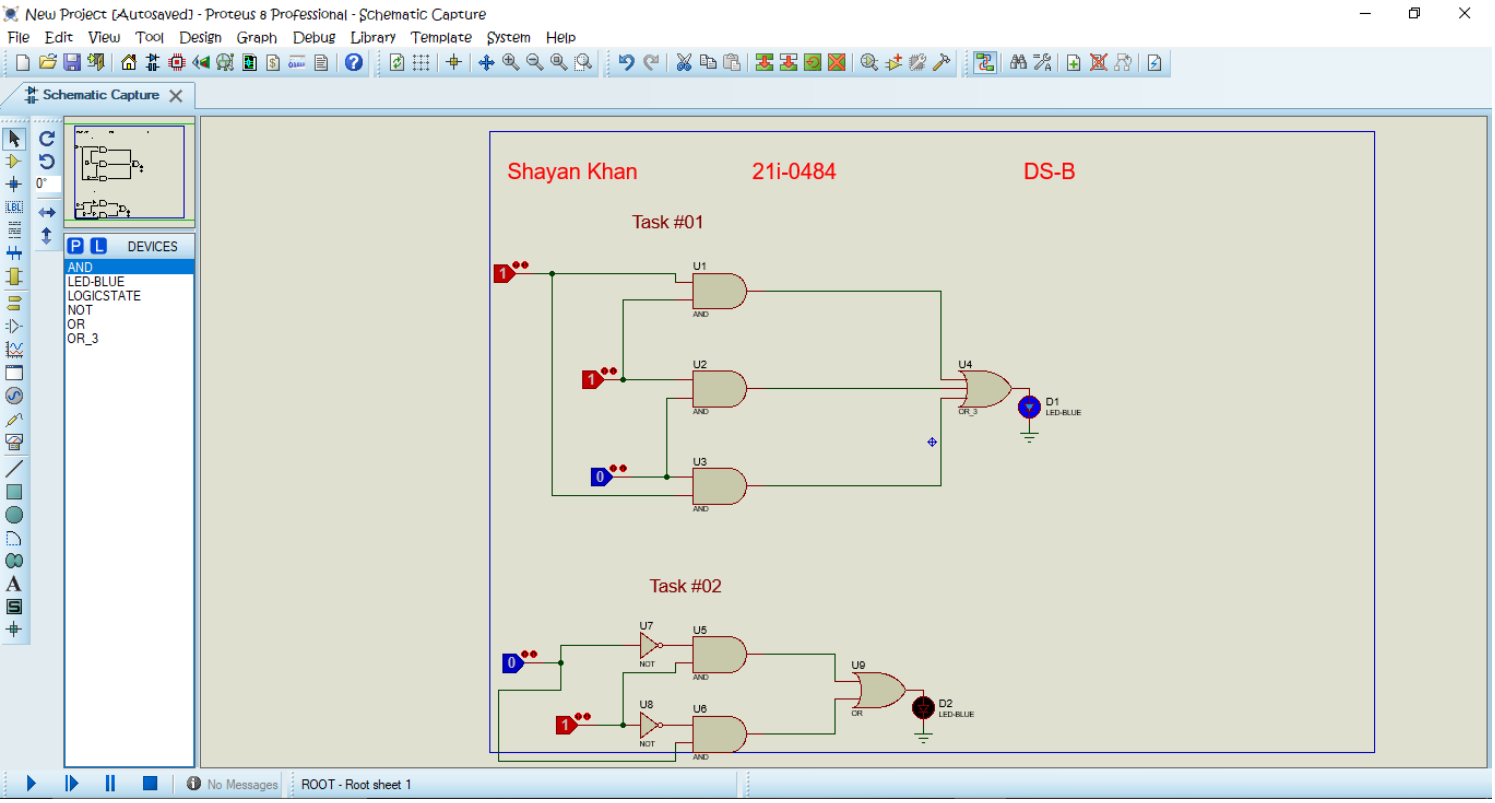

DIGITAL LOGIC TRAINING SYSTEM
IT-300
LOGIC SWITCHES
PUSH SWITCHES
STATE MONITOR
DIGIT-2
DIGIT-1
CLOCK GENERATOR
POT.1 10K
POT.2 1K
MIN
MAX
LOGIC PROBE
HIGH
LOW
PULSE
FIXED POWER SUPPLIES
+5V
+15V
GND
-15V

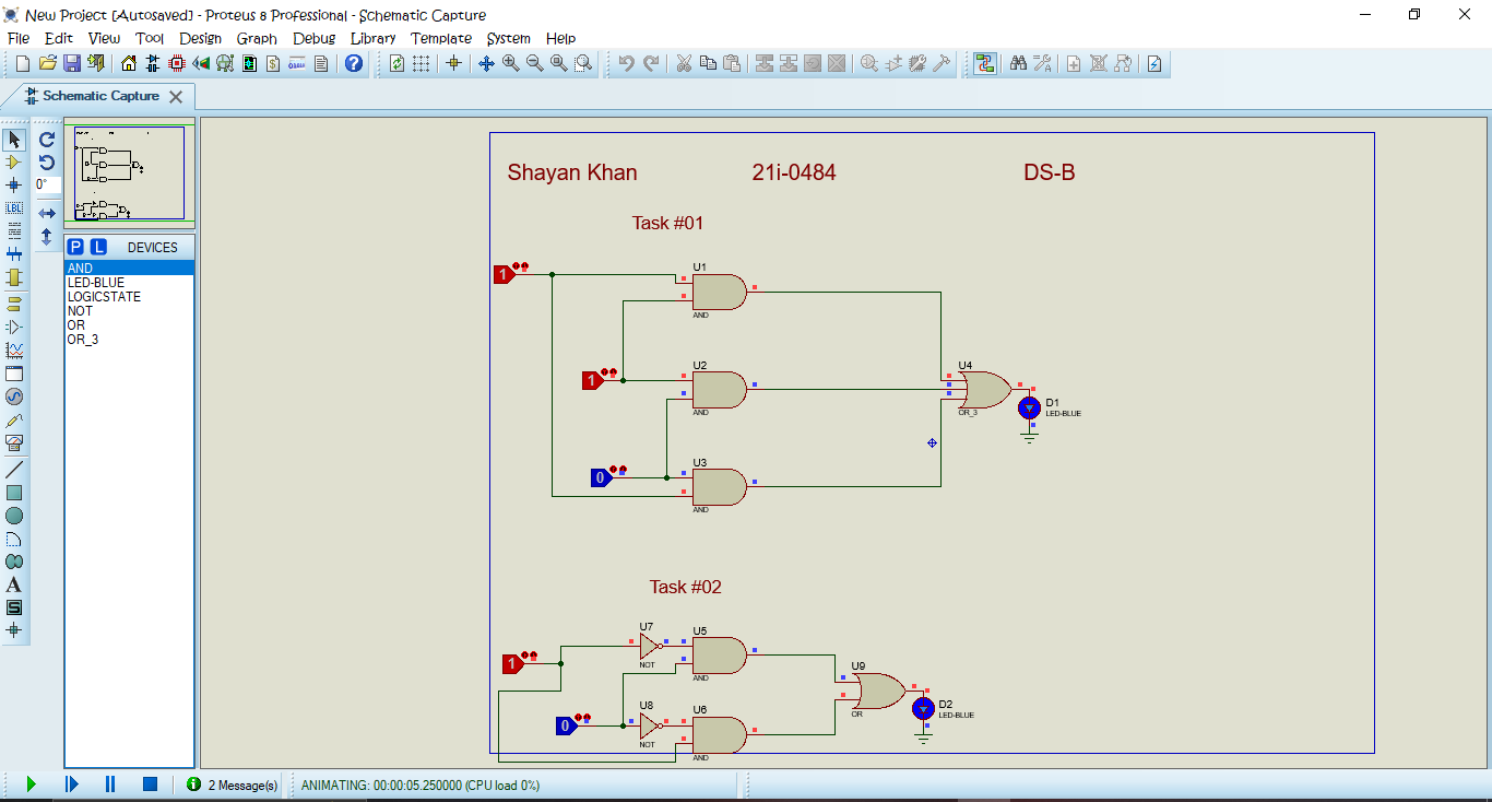
TASK #02

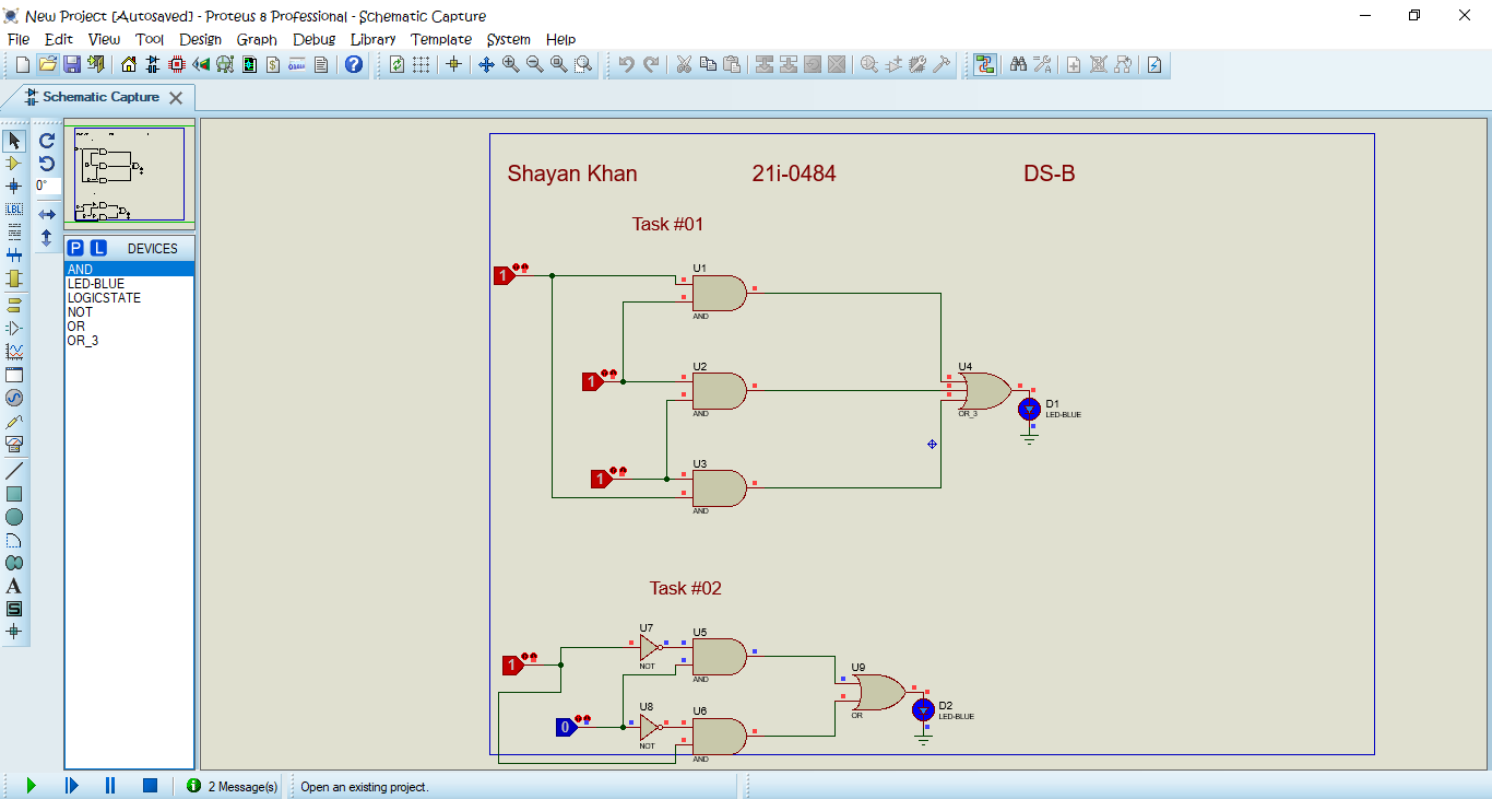

LOGIC SWITCHES
STATE MONITOR
DIGIT-2
DIGIT-1
POT.1 10K
POT.2 1K
MIN
MAX
CLOCK GENERATOR
FIXED POWER SUPPLIES
+5V
+15V
GND


DIGITAL LOGIC TRAINING SYSTEM
IT-300
LOGIC SWITCHES
PUSH SWITCHES
STATE MONITOR
DIGIT-2
DIGIT-1
POT.2 1K
MIN
MAX
CLOCK GENERATOR
RANGE
OUTPUT
LOGIC PROBE
HIGH
LOW
PULSE
FIXED POWER SUPPLIES
+5V
+15V
GND
-15V

PROTEUS IMPLEMENTATION


New Project [Autosaved] - Proteus 8 Professional - Schematic Capture
File Edit View Tool Design Graph Debug Library Template System Help
Schematic Capture
DEVICES
AND
LED-BLUE
LOGICSTATE
NOT
OR
OR_3
Shayan Khan
21i-0484
DS-B
Task #01
U1
U2
U3
U4
D1
LED-BLUE
Task #02
U7
U8
U5
U6
U9
D2
LED-BLUE
No Messages
ROOT - Root sheet 1


New Project [Autosaved] - Proteus 8 Professional - Schematic Capture
File Edit View Tool Design Graph Debug Library Template System Help
Schematic Capture
DEVICES
AND
LED-BLUE
LOGICSTATE
NOT
OR
OR_3
Shayan Khan
21i-0484
DS-B
Task #01
U1
U2
U3
U4
D1
LED-BLUE
Task #02
U7
U8
U5
U6
U9
D2
LED-BLUE
2 Message(s)
ANIMATING: 00:00:05.250000 (CPU load 0%)


New Project [Autosaved] - Proteus 8 Professional - Schematic Capture
File Edit View Tool Design Graph Debug Library Template System Help
Schematic Capture
DEVICES
AND
LED-BLUE
LOGICSTATE
NOT
OR
OR_3
Shayan Khan
21i-0484
DS-B
Task #01
U1
U2
U3
U4
D1
LED-BLUE
Task #02
U5
U6
U7
U8
U9
D2
LED-BLUE
2 Message(s)
Open an existing project.